

EECS 290

Spring 2019

APRIL 8 Lecture

Half Bridge Converter

Outline

Basic Power Converter Components - terminology

Ideal half bridge converter

- basic architecture
- switched model
- averaged model

Non-ideal half bridge

- what's different?
- Averaged model

Half Bridge control

- control model
- basic control design: current tracking
- Feed forward compensation
- Sinusoidal command following

Objectives

1. Understand basic converter architecture design principles
2. Understand averaged models - ideal and non-ideal converter
3. Understand basic control loop design principles

Design factors

- a. Bandwidth / response time
- b. Startup current
- c. Rejecting AC-side disturbances

Switch types

"Uncontrollable switch" The diode $\xrightarrow{i \text{ (forward direction)}}$

- Allows current flow in forward direction

(voltage drop from + to - terminal)

- Prevents current in reverse direction

(but not if voltage exceeds "breakdown voltage")

"Semi-controllable switch" : Thyristor a.k.a. Semi-controllable Rectifier (SCR)

- insulates up to point a signal is applied


- continues conducting until conditions in circuit cause it to stop.

- Most common in high power (transmission scale) applications)

Switch Types, ctd


"Fully controllable switches" : (Transistors)

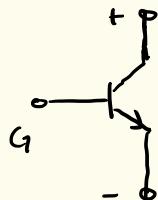- Gating command determines both ON and OFF state.
- More common in power applications: Insulated Gate Bipolar transistor: IGBT - (3 layer)



- + low control power
- + high frequency
- high on-state losses
- + high lifetime

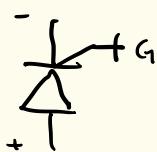- Less common: Insulated Gate Conducting Transistor IGCT (4 layer)




- + high tolerance for overload
- + low on-state losses
- cooling problems

Switch Classification

In converters, to my knowledge, we focus on

"reverse conducting" switches:

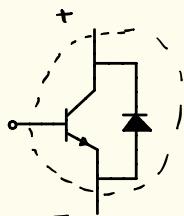

why do this?

- IGBT don't tolerate high reverse voltage
- The diode protects it

Converter Types: Current Source vs. Voltage Source

This classification refers to operating characteristics of the DC source. [1st discuss green, then red]

CSC: Typically DC source in series with a large


inductor



← Commercial switches
limited availability,
so CSC less common


VSC: DC source typically in parallel with a large

capacitor

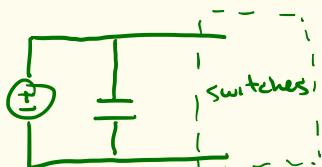

← This is the more common power converter. Based on IGBT.

DC/AC Half Bridge Converter Structure

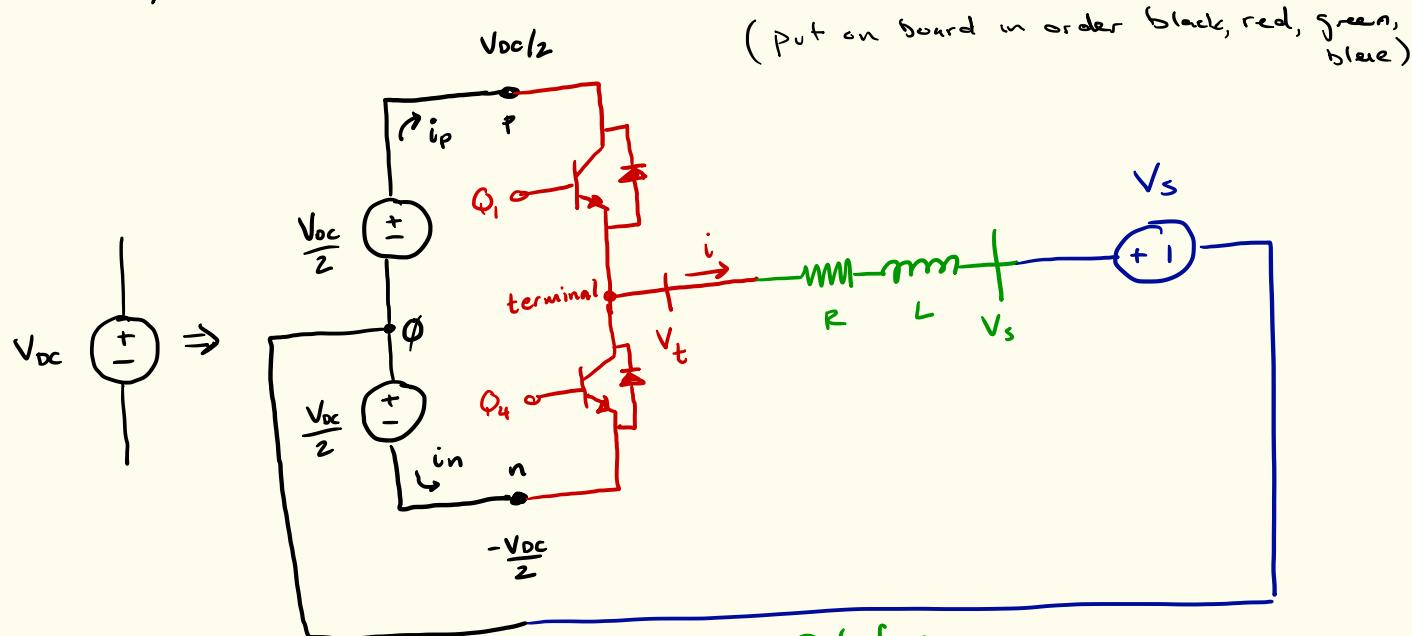

DC side

- Terminal ϕ is the "midpoint"

Converter

- V_t , terminal voltage, $\{\frac{V_{dc}}{2}, -\frac{V_{dc}}{2}\}$
- V_t has "ripple"

Interface reactor


- Acts as filter on V_t ripple
- Also provides $(V_t - V_s)$, which is key control variable

AC side

- V_s is AC voltage source

Switch Control: Pulse Width Modulation

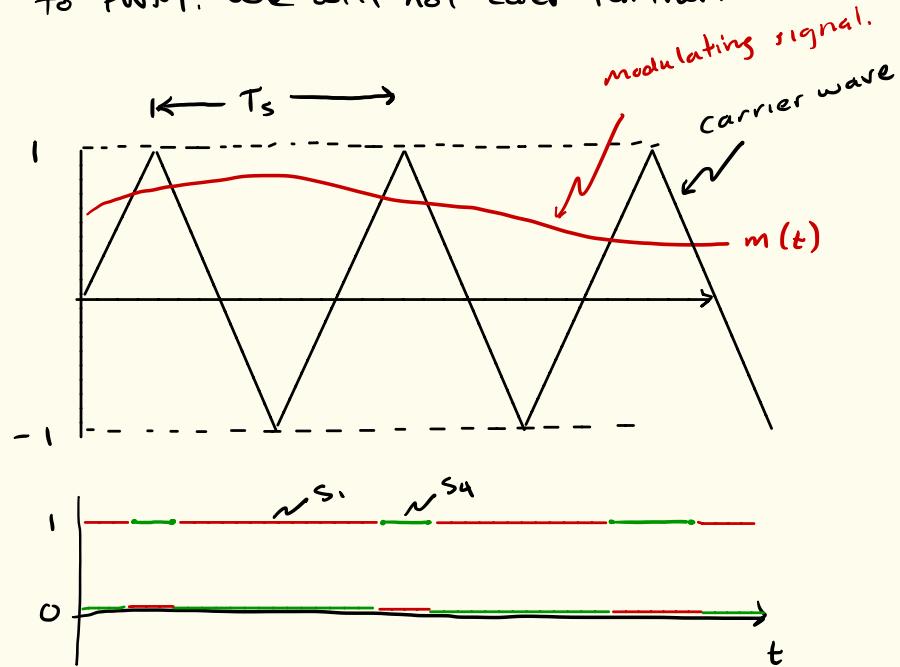- Note, Seth talked about digital control as an alternative to PWM. We will not cover further.



Important: All signals here are digital

carrier < modulating

$$\Rightarrow s_1 = 1$$

$$s_4 = 0$$

carrier > modulating

$$\Rightarrow s_1 = 0$$

$$s_4 = 1$$

T_s : Typically $0(100\mu\text{s})$
 $\sim 0(1,000 \text{ Hz})$

Switch Control analysis

Assumptions

1. Diodes & transistors perfect short circuits when conducting
2. " " " open circuit " blocking
3. No "turn off current"
4. Instant transitions from conducting to blocking
5. AC-side i is "ripple free", and DC over T_s time scale.


Last assumption can be justified on grounds that inductance between V_t & V_s is sufficiently high to prevent fast current changes.

Switch Control Analysis, ctd

Let

$i > 0$ (AC-side current +ive):

$$s_1 = 0, s_4 = 1$$

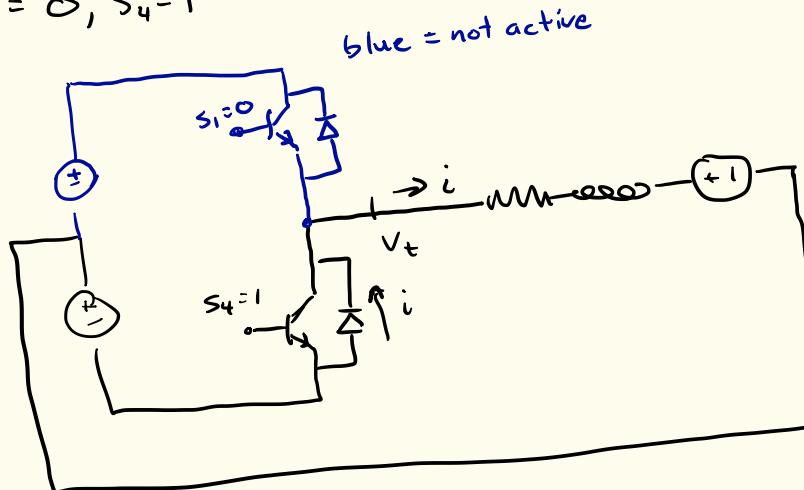

In this case,

$$V_t = -\frac{V_{dc}}{2}$$

- For $i > 0$, $s_1 = 1$, $s_4 = 0$, $\Rightarrow V_t = +\frac{V_{dc}}{2}$. Current won't flow through s_4 , the active leg moves to the top.

Converter Switched Model

Let

$$s_1(t) + s_4(t) \equiv 1$$

$$\Rightarrow v_t(t) = \left(\frac{V_{DC}}{Z} \right) s_1(t) + \left(-\frac{V_{DC}}{Z} \right) s_4(t)$$

$$i_p(t) = i s_1(t)$$


$$i_n(t) = i s_4(t)$$

$$P_{DC}(t) = \left(\frac{V_{DC}}{Z} s_1(t) - \frac{V_{DC}}{Z} s_4(t) \right) i = \underbrace{\frac{V_{DC}}{Z} (s_1(t) - s_4(t))}_\text{negative when s_4 is on} i$$

(remember we are assuming $i = \text{constant}$)

AC Side Current Dynamics

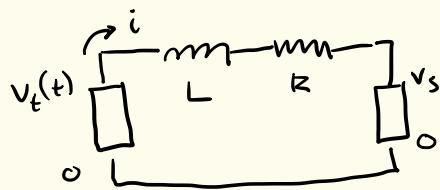This will be useful for averaging, up next.



$$\text{KVL: } L \frac{di}{dt} + Ri = V_t(t) - V_s$$

R
For now, assume constant.

Converter Averaged Model

- Why do we average?

- Simplifies analyses

- Compensators & filters in control system typically
act as low pass

Let

$$\begin{aligned} V_t(t) &= \frac{1}{T_s} \int_{t-T_s}^t V_t(\tau) d\tau + f(t) \\ &\quad \uparrow \\ &\quad \text{zero mean, high frequency stuff} \\ &= \bar{V}_t(t) + f(t) \end{aligned}$$

$$\Rightarrow L \frac{di}{dt} + Ri = \bar{V}_t(t) + f(t) - V_s$$

Converter Averaged Model, continued

since the equation is linear,

$$L \frac{d\bar{i}}{dt} + R\bar{i} = \bar{V}_t - V_s \quad ; \quad L \frac{d\tilde{i}}{dt} + R\tilde{i} = f(t)$$

$$i = \bar{i} + \tilde{i}$$

\uparrow
ripple

If frequency of $f(t)$ is high relative to $\frac{R}{L}$,

$$\tilde{i} \approx 0 \Rightarrow i \approx \bar{i}$$

Converter Averaged Model, continued

Let d = "Duty cycle" for s_1 (fraction of T_S that $s_1 = 1$)

$$\Rightarrow \bar{s}_1(t) = d$$

$$\bar{s}_4(t) = 1 - d$$

Assumption: m varies much more slowly than carrier

$$\Rightarrow \bar{V}_{DC} = \text{constant over } T_S.$$

(Finally) Averaged Quantities

Remember,

$$v_t(t) = \frac{V_{DC}}{2} s_1(t) - \frac{V_{DC}}{2} s_2(t)$$

$$\Rightarrow \bar{v}_t = \frac{V_{DC}}{2} d - \frac{V_{DC}}{2} (1-d) = d V_{DC} - \frac{V_{DC}}{2}$$

$$= \left(d - \frac{1}{2}\right) V_{DC}$$

$$= m \frac{V_{DC}}{2} \quad (m \text{ is the value of the modulating wave}).$$

also, $\bar{i}_p = \frac{1+m}{2} i$ $\bar{i}_n = \frac{1-m}{2} i$

r

+ive side
current

f

-ive side
current

Remember, we assume $i = \text{constant over } T_s$ time scale.

Example (put on board in order black, red, green, orange)

$$L = 690 \mu\text{H}$$

$$R = 5 \text{ m}\Omega$$


$$\frac{V_{DC}}{2} = 600 \text{ V, initially}$$

$$V_s = 400 \text{ V, initially}$$

$$m = 0.68, \text{ initially}$$

$$f_s = 1620 \text{ Hz}$$
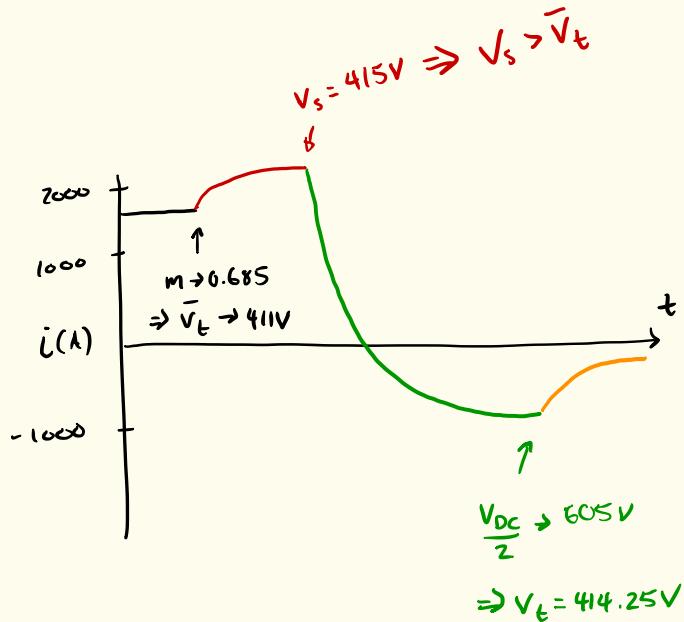
$$\Rightarrow \bar{V}_t = 408 \text{ V, initially}$$




Non-ideal converter

Previous model used "ideal" switch model

Here is a schematic of an alternative:


New assumptions (class to provide)

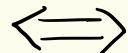1. Each switch is modeled by a voltage drop in series w/a resistance



2. Transistors turn on immediately, but turn-off experiences a "tailing current"

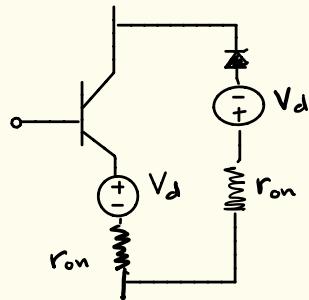3. Diodes experience "reverse current recovery"



Voltage model for non-ideal converter

$$\bar{V}_t' = \frac{m V_{DC}}{2} - \frac{i}{l_{il}} V_e - r_e i$$

$$V_e = V_d - \left(\frac{Q_{rr} + Q_{rec}}{T_s} \right) r_{on} + V_{DC} \frac{t_{rr}}{T_s}$$

Annotations:

- charge associated w/ diode reverse recovery
- charge associated w/ transistor tailing current
- reverse recovery duration
- drop across switch
- switch resistance

$$r_e = \left(1 - \frac{t_{rr}}{T_s} \right) r_{on}$$

Power loss for non-ideal converter

Ideal converter had zero loss

Non-ideal, as modeled here, has

$$\overline{P}_{\text{loss}} = V_{\text{DC}} \left(\frac{Q_{rr} + Q_{tc}}{T_s} \right) + V_e |i| + r_e i^2$$

\Rightarrow zero current still experiences losses, and losses grow with V_{DC}

\Rightarrow But at nonzero currents, increasing V_{DC} (for a given power delivery)

will reduce losses by decreasing current.

Half bridge model recap

- Current to AC side assumed constant over switching period due to inductance in "interface reactor" / AC source
- Modulation impacts average voltage. Even if current experiences voltage rise for a fraction of cycle, if it experiences voltage drop for a larger fraction, the average power will be into the device
- Averaging provides simple formulae based on m (carrier wave value) for voltage and current
- Non-ideal converter model introduces no additional dynamics, just different voltages due to losses.


Half Bridge control model

From here on, $\bar{\cdot}$ (overbar) are d. pped, but quantities are averaged unless otherwise noted

$$\left[\frac{di}{dt} + (R + r_{on})i = V_t - V_s \right] \Rightarrow$$


↑
device resistance included

implicitly includes device voltage drop

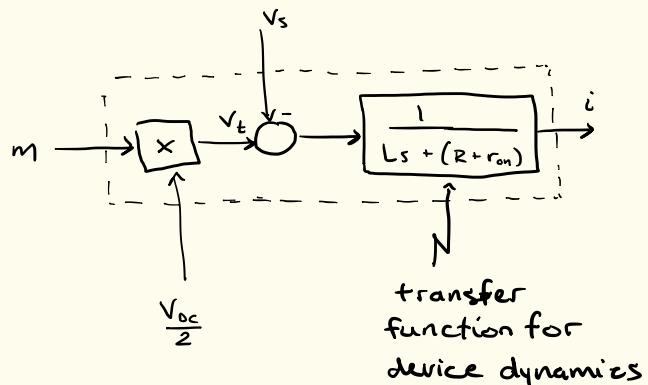

The V_d (device voltage drop) is omitted because it is independent of current - but measurement at the actual terminal would need to compensate.

Half Bridge Control - current control

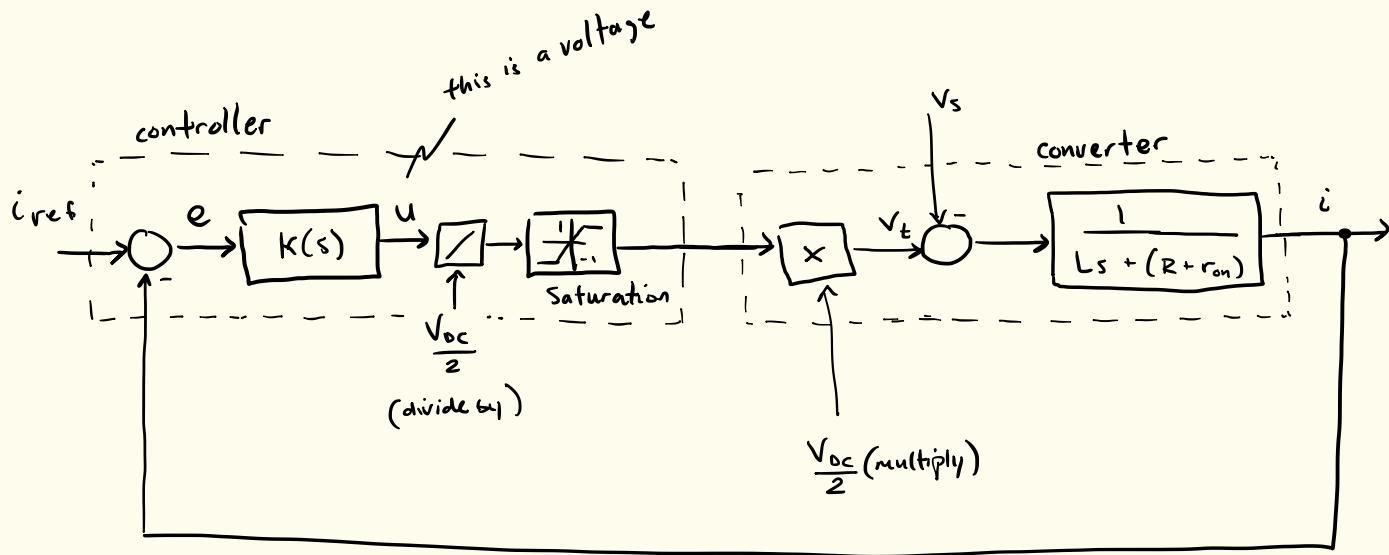

e : current error

$K(s)$: compensator. We're about to talk about what is in here

V_{dc} must be sensed if there are DC-side dynamics.

Control design

PI control works well for some cases (in text, step changes are the initial focus)

$$\Rightarrow K(s) = k_p + \frac{k_i}{s} = \frac{k_p s + k_i}{s}$$

↑
ensures zero error tracking

$$\Rightarrow \text{loop gain } l(s) = \frac{k_p}{Ls} \left(\frac{s + \frac{k_i/k_p}{s}}{s + \frac{R+r_{on}}{L}} \right)$$

zeros are roots to numerator.

poles are roots to denom.

(aside, $= K(s) G(s)$)
closed loop xfr f'n)

Basic control Design

- (1), note that pole $p = -(R + r_{on})/L$ is stable.
You can also see this from time domain ODE .
- Second, improve response by setting zero equal to pole

$$\Rightarrow \frac{k_i}{k_p} = \frac{R + r_{on}}{L}$$

- Third, tune desired time constant of response. How should we think about this?

\Rightarrow make sure response is significantly slower than switching period

Control Design, etc.

Closed loop time constant is $\tau_i = \frac{L}{k_p}$. Typical to set this as $10 \times$ switch frequency,

E.g., Switching frequency 1620 Hz $\Rightarrow \tau_i = 6.2 \text{ ms}$

Closed-loop transfer function

$$G_i(s) = \frac{i(s)}{i_{ref}(s)} = \frac{1}{\tau_i s + 1}$$

\Rightarrow 1st order current dynamics.

Example

$$L = 690 \mu\text{H}$$

$$R = 5 \text{ m}\Omega$$

$$r_{on} = 0.88 \text{ m}\Omega$$


$$V_d = 1.0 \text{ V}$$

$$\frac{V_{DC}}{2} = 600 \text{ V}$$

$$V_s = 400 \text{ V DC}$$

$$f_s = 1620 \text{ Hz.}$$



(start with black axes and red i_{ref})

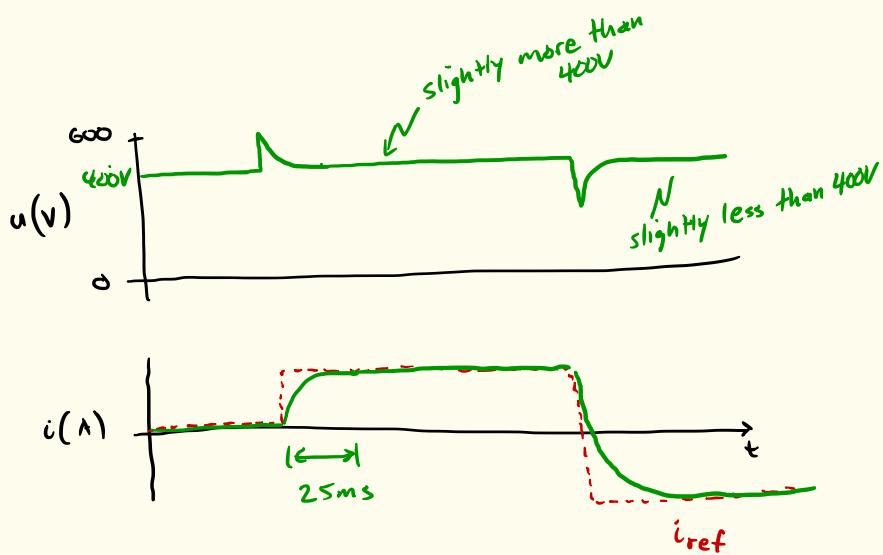

$$\text{Aim for time } \Rightarrow k_p = 0.138 \Omega \\ \text{const } 5 \text{ ms} \quad k_i = 1.176 \Omega$$


Startup Transients

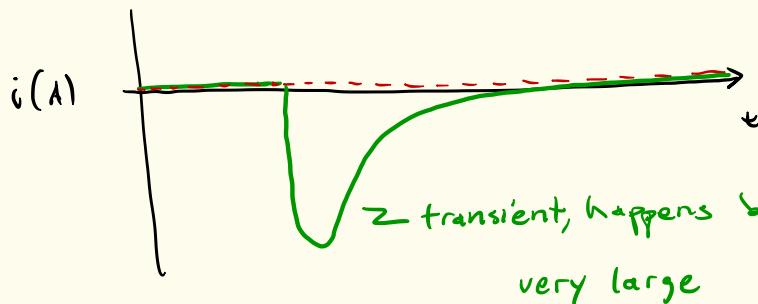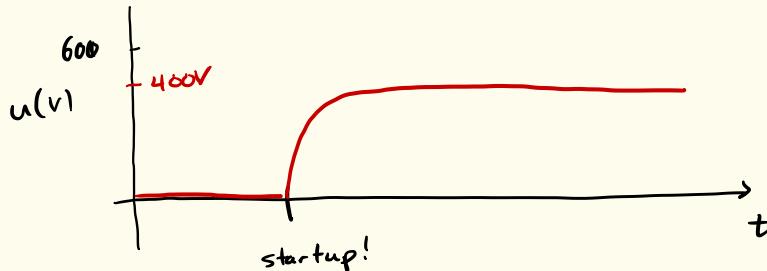Suppose converter begins zero current operation with $m=0$
and $i_{ref} = 0$



Feed Forward Compensation

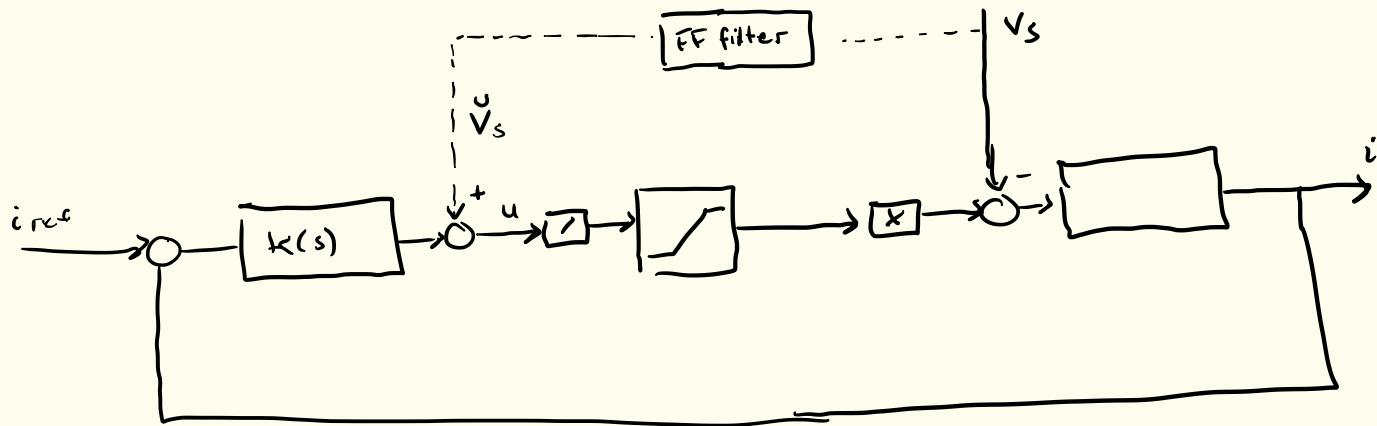Solution to startup transient (and other problems):



- Add (filtered) measure of $V_s \Rightarrow$ initial voltage difference is zero
- Compensator now produces deviation from V_s required to reach i_{ref} .

Feed Forward Control etc.

Why else might feed forward compensation be beneficial?

What happens if V_s is time-varying?


⇒ FF compensation also helps to follow time-varying
AC dynamics

Sinusoidal Command Following

To this point we have not discussed sinusoidal AC sources. Let's do that now.

$$i_{ref} = \hat{I} \cos(\omega_0 t + \phi)$$
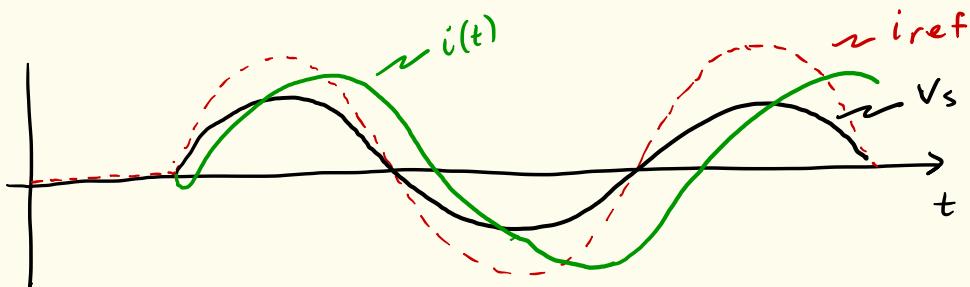
$$\text{with } G_i(s) = \frac{i(s)}{i_{ref}(s)} = \frac{1}{\tau_i s + 1} \quad (\text{from before, no ff comp.})$$



Sinusoidal, ctd ...

So the current out is lower and later:

$$i(t) = \frac{\hat{I}}{\sqrt{1 + (\tau_i/\omega_0)^2}} \cos(\omega_0 t + \phi + \delta)$$
$$\delta = -\tan^{-1}(\tau_i \omega_0)$$

$$\tau_i = 2 \text{ ms}, 60 \text{ Hz} \rightarrow$$

- Amplitude is 80% of \hat{I} , and
- δ is 37°

Sinusoidal, etc

- There are a few ways to improve tracking, and textbook covers in detail how to design $K(s)$ to do this.
- But for 3ϕ systems we can work in d-q coordinates - a much simpler proposition since control variables become DC quantities.

Takeaways