

EECS 2900

Spring 2019

APRIL 15 Lecture

Three Phase VSCs.

Announcements

- Next week

- YI ch 8: dq control
- Ramasubramanian

- Last week of Class

Cancelled → go to Amber kinetics!

- Reading week

- Markwick Lin present
- Review Rocabert et al.



- Final project

- I will post guidelines this week.

Today

- Half bridge examples
- Two-level 3Ø VSC
 - Architecture
 - Average model
 - Switched model
 - dq representation
- 3-level "neutral point clamped" 3Ø VSC
 - Architecture
 - Average model
 - Switched model
 - dq representation
- Generic model of both for control representations
- Key takeaways
 - These are very easy to understand at their core
 - In terms of dynamics, not much happening here w/o control

Half Bridge review.

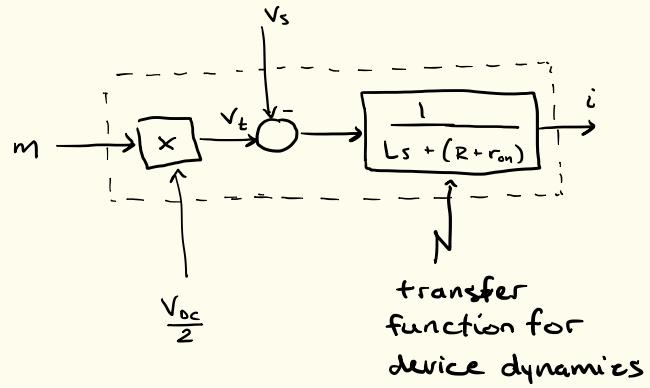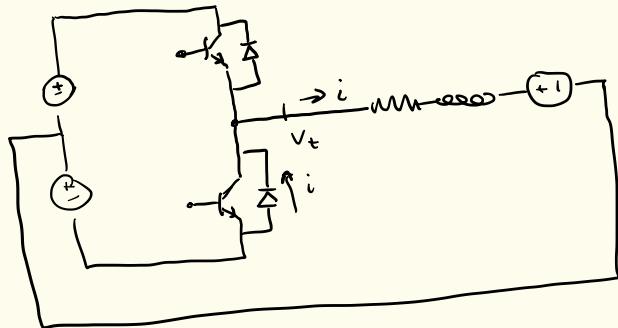

Example (put on board in order black, red, green, orange)

$$L = 690 \mu\text{H}$$

$$R = 5 \text{ m}\Omega$$


$$\frac{V_{DC}}{2} = 600 \text{ V, initially}$$

$$V_s = 400 \text{ V, initially}$$


$$m = 0.68, \text{ initially}$$

$$f_s = 1620 \text{ Hz}$$
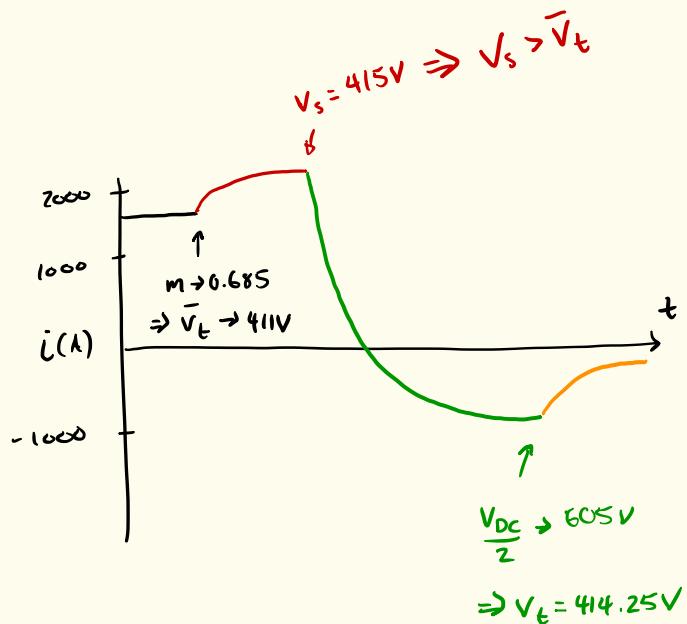
$$\Rightarrow \bar{V}_t = 408 \text{ V, initially}$$



I_Z Bridge control, reminder

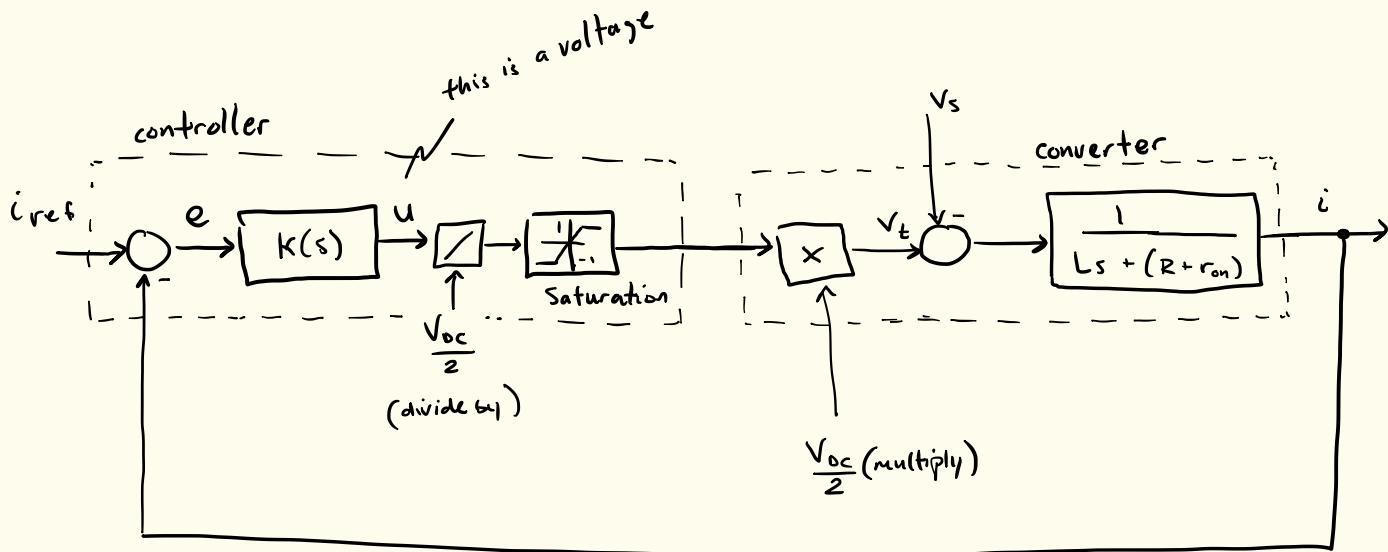

- We tune $K(s)$ to quickly reject disturbances to i .

Example

$$L = 690 \mu\text{H}$$

$$R = 5 \text{ m}\Omega$$

$$r_{on} = 0.88 \text{ m}\Omega$$

$$V_d = 1.0 \text{ V}$$


$$\frac{V_{DC}}{2} = 600 \text{ V}$$

$$V_s = 400 \text{ V DC}$$


$$f_s = 1620 \text{ Hz.}$$

Aim for time $\Rightarrow k_p = 0.138 \Omega$
const 5ms $k_i = 1.176 / \Omega$


(start with black axes and red i_{ref})

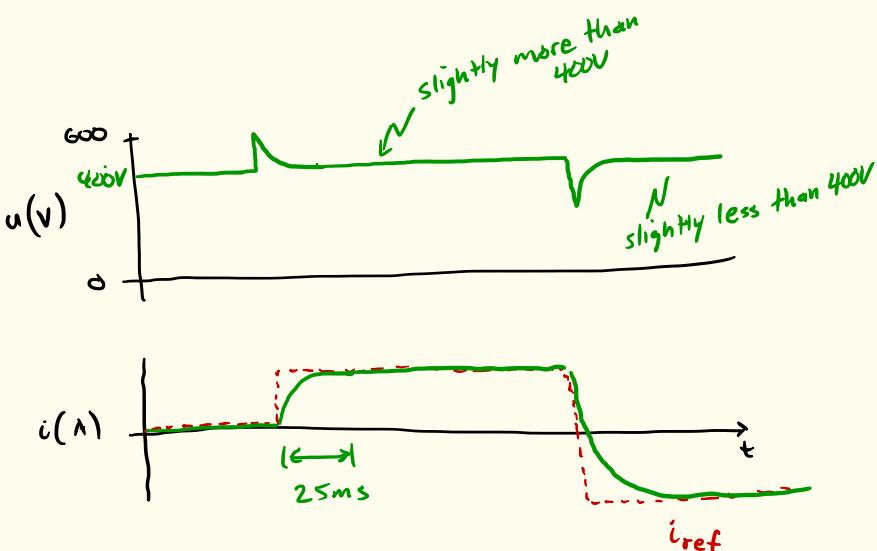

2-Level 3 ϕ VSC architecture (sin 5.2.1)

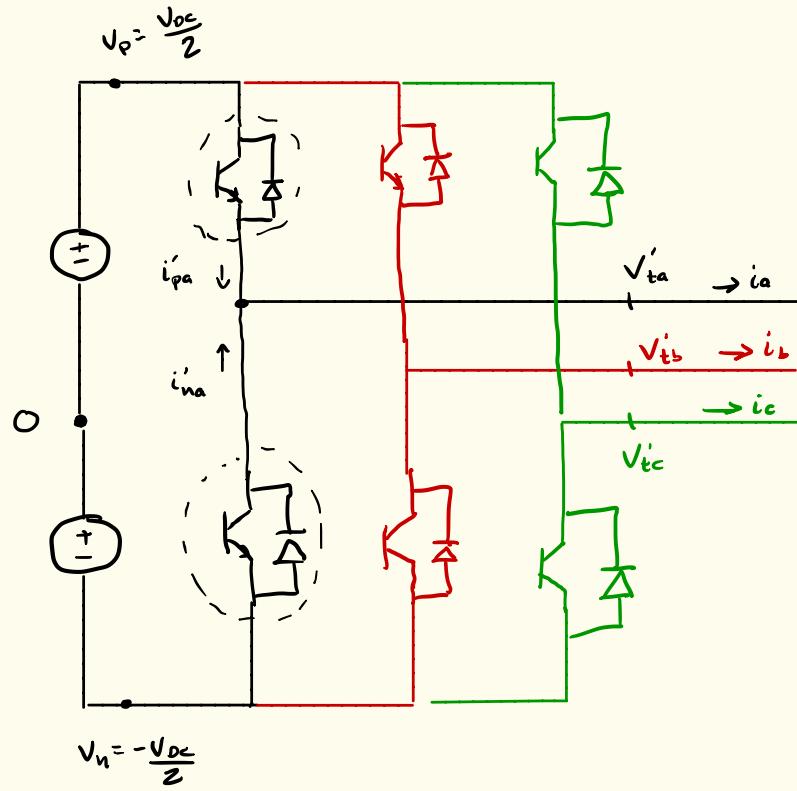

As before, switches are non-ideal

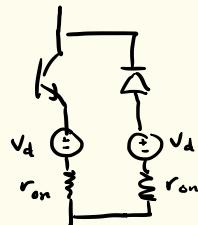

Averaged model from last time

Single half bridge, from last time - averaged, nonideal

$$V'_t(t) = m(t) \frac{V_{DC}}{2} - \frac{i(t)}{|i(t)|} V_e - r_e i(t)$$

↑
modulating
signal

↑
Voltage offset
due to semiconductor
drop and post-switch
dynamics.

Challenge with the voltage offset

- It has a nonlinear effect on the voltage-current relationship when i goes thru zero. \Rightarrow distortion in $V'(t)$
- But $V_e \ll V'(t)$ and controllers remove much of the distortion \Rightarrow ignore

3Φ model (sin 5.2.2)

$$v'_{ta}(t) = m_a(t) \frac{V_{oc}}{2} - r_{on} i_a(t)$$

$$v'_{tb}(t) = m_b(t) \frac{V_{oc}}{2} - r_{on} i_b(t)$$

$$v'_{tc}(t) = m_c(t) \frac{V_{oc}}{2} - r_{on} i_c(t)$$

} phase currents and phase switching strategy dictate voltage.

Question: If m_a, m_b, m_c are balanced control signals, is current balanced?

Answer: Not if the system the device is connected to is unbalanced.

Losses - one leg (sin 5.2.3)


$$P_{\text{loss}} = V_{\text{DC}} \left(\frac{Q_{rr} + Q_{tc}}{T_s} \right) + V_e l i_l + r_e i^2$$

Q: Which terms matter at low current? Which matter at high current?

A: The second and third terms will go away at zero current, but the first will not. \Rightarrow poor low-load efficiency.

- Losses for 3D converter simply 3X this.

Losses - a little more

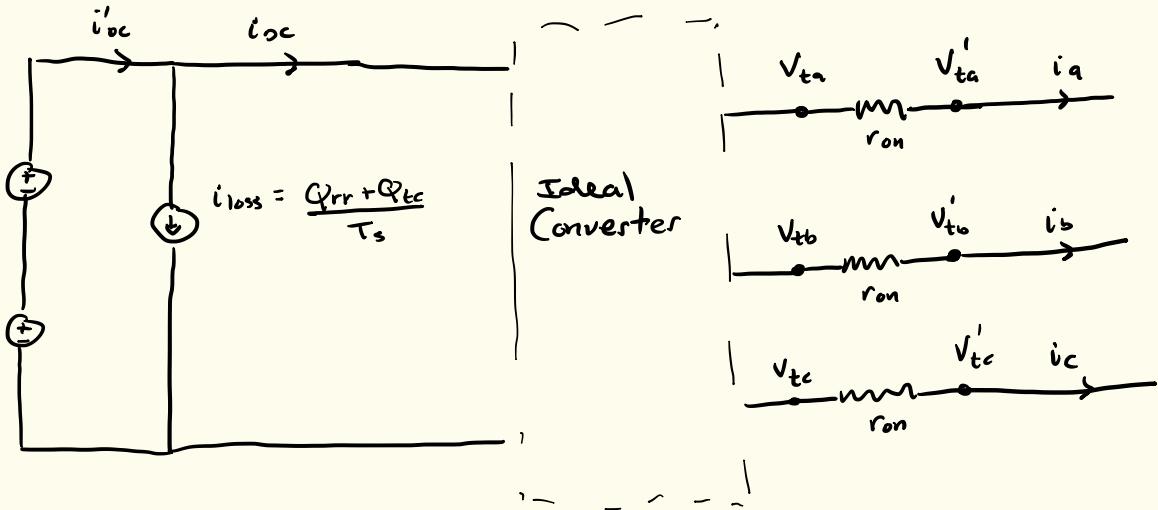

It's typical to lump i_{loss} , r_{on} in to DC and AC systems, respectively. \Rightarrow leave them out from further model developments.

Working model for 2-level 3Ø

$$V_{ta}(t) = m_a(t) \frac{V_{dc}}{2} , \quad m_a(t) = \hat{m}(t) \cos(\varepsilon(t))$$

we'll discuss this soon.

$$V_{tb}(t) = m_b(t) \frac{V_{dc}}{2} , \quad m_b(t) = \hat{m}(t) \cos(\varepsilon(t) - 2\pi/3)$$

$$V_{tc}(t) = m_c(t) \frac{V_{dc}}{2} , \quad m_c(t) = \hat{m}(t) \cos(\varepsilon(t) - 4\pi/3)$$

Q: Suppose there is a sharp decline in AC-side voltage. What dynamics will ensue in this model?

A: we don't have enough information...

- The model doesn't describe the control loops that influence $m(t)$
- The model assumes V_{dc} is fixed. In general this is not true...

Non-constant V_{DC}

- The value of V_{DC} need not be constant if it is sensed and passed into the controller.
- But one needs to at least be aware of
 - * The time constant of the voltage sensor (likely very small)
 - * Any dynamics that might be present on the DC side \Rightarrow account for those dynamics in controller design.

Space Phasors and α_B (4.42)

Suppose you have a balanced 3 ϕ quantity

$$f_a + f_b + f_c = 0$$

$$\vec{f}(t) = \frac{2}{3} \left(e^{j\omega} f_a(t) + e^{j2\pi/3} f_b(t) + e^{j4\pi/3} f_c(t) \right)$$

= space phasor.

α_B coord is simply a decomposition into real and imag. parts

$$\vec{f}(t) = f_\alpha(t) + j f_\beta(t)$$

One can show

$$\begin{bmatrix} f_\alpha \\ f_\beta \end{bmatrix} = \frac{2}{3} \begin{bmatrix} 1 & -1/2 & -1/2 \\ 0 & \sqrt{3}/2 & -\sqrt{3}/2 \end{bmatrix} \begin{bmatrix} f_a \\ f_b \\ f_c \end{bmatrix} = 2/3 C \begin{bmatrix} f_a \\ f_b \\ f_c \end{bmatrix}$$

Two Level VSC in $\alpha\beta$ (5.3.2)


$$\vec{V}_t(t) = \vec{m}(t) \frac{V_{oc}}{2} \Rightarrow V_\alpha(t) + jV_\beta(t) = \left[m_\alpha(t) + j m_\beta(t) \right] \frac{V_{oc}}{2}$$



In (assumed) balanced conditions,
we can represent 3 ϕ time varying
quantities with just two time-varying.

$\alpha\beta$ control (5.3.2)

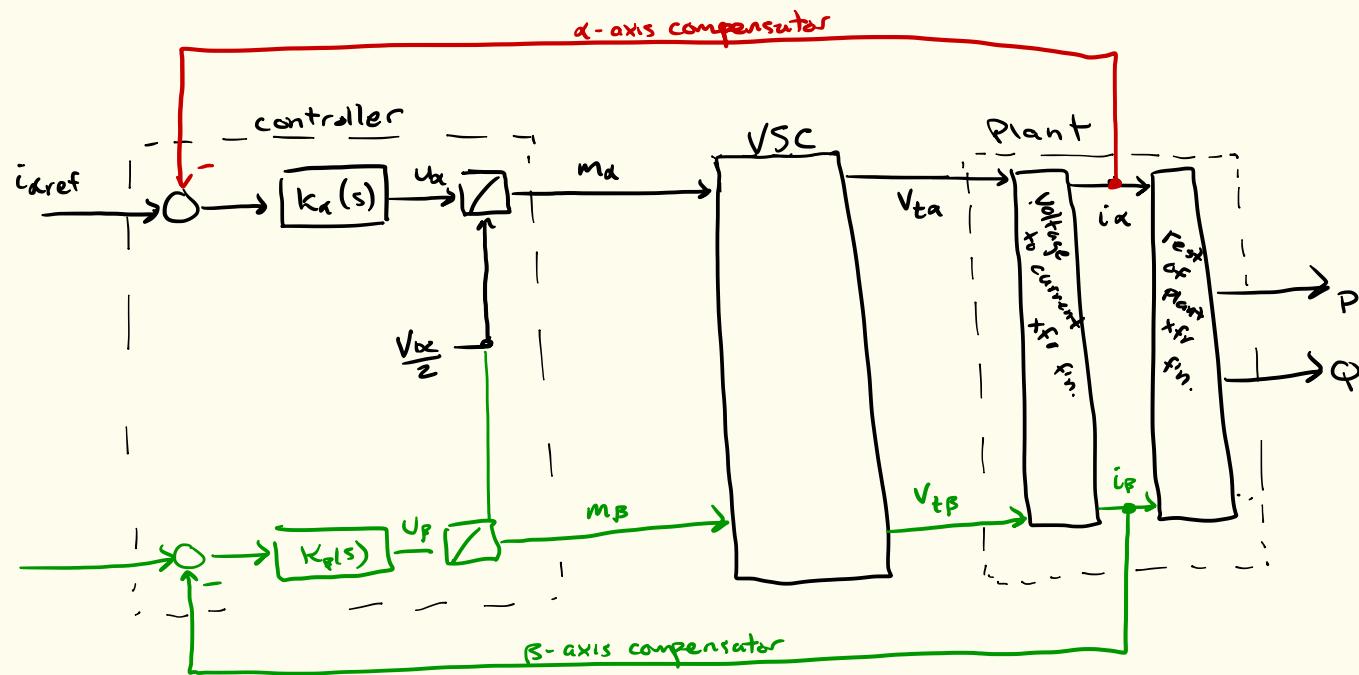Current control is frequently used as a means to another end (real power, frequency, and so on). So it's a good starting block.



Quick note on control

- P and Q might be the ultimate control objectives
- Therefore there would be an "outer control loop" that feeds P+Q errors back in to current references.

dq representation in 5.3.3.

Remember we had

$$V_{ta}(t) = \hat{m}(t) \cos(\varepsilon(t)) \frac{V_{dc}}{2}, \text{ and more for phase } b \neq c,$$

$$\varepsilon(t) = \omega t - \Theta_0$$

↑
frequency ↑
phase

dq transform is

$$f_d + j f_q = (f_d + j f_q) e^{-j\varepsilon(t)} \Rightarrow \vec{f}(t) = (f_d + j f_q) e^{j\varepsilon(t)}$$

i.e., we just phase shift by an amount dictated by frequency & phase of the sinusoid.

dq representation, continued

As we've discussed a few times already, d- and q-components are constant if

- system is balanced
- you've got the right representation of $\varepsilon(t)$.


$$(V_{td} + jV_{tq}) e^{j\varepsilon(t)} = \frac{V_{dc}}{2} (m_d - j m_q) e^{j\varepsilon(t)}$$

$$\Rightarrow V_{td} = m_d \frac{V_{dc}}{2}$$

$$V_{tq} = m_q \frac{V_{dc}}{2}$$

Issues with the two-level 3Ø converter

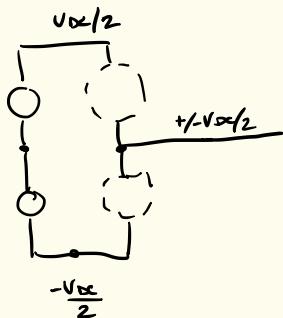- Each switch cell withstands entire DC-side voltage when off



⇒ need high voltage ratings
for high DC-side voltage.
May not be possible for some
applications

- Require relatively large LC filters due to high output distortion
- Switching losses high due to relatively fast switch frequency required.

Solving 2-level 3 ϕ problems

- Connect multiple switches in series
 - * but might be hard to gate with perfect timing
- 3-level neutral point clamped enables similar benefits without as many series connections


3-level Neutral point clamp (NPC)

3-level: can produce 3 voltage levels

NPC : DC-side neutral point is exposed to the middle of
the switched circuit


- In what follows I'll make drawings w/o a return path.
- Don't worry, all we care about now is how to produce different voltages.
- Eventually a 3 ϕ circuit will produce return - but that comes later.

What voltage?

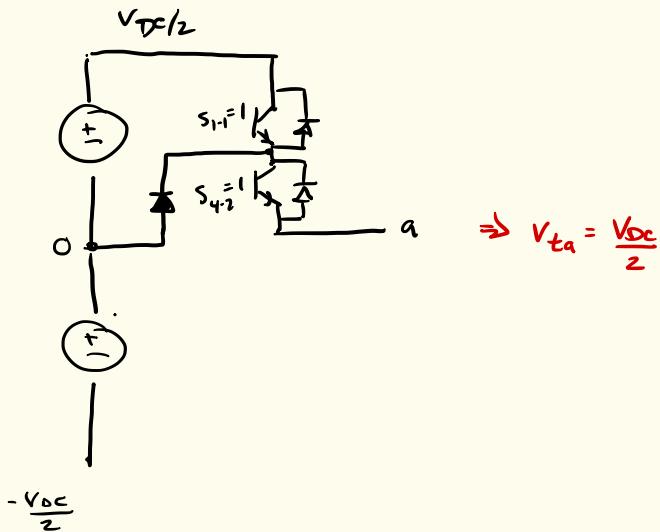

Positive: Neutral clamp diode keeps neutral voltage from appearing


What voltage?

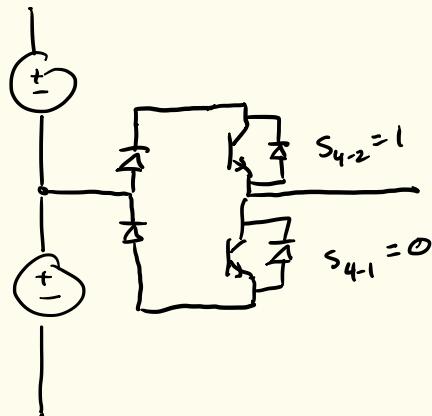

$$\Rightarrow V_{ta} = 0$$

A: Zero



What voltage?

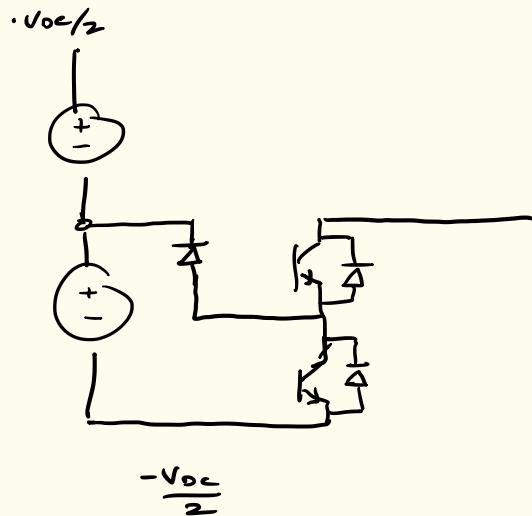

$$V_{ta} = -\frac{V_{dc}}{2}$$

Negative voltage. Again,
neutral clamp diode keeps
0V from appearing.

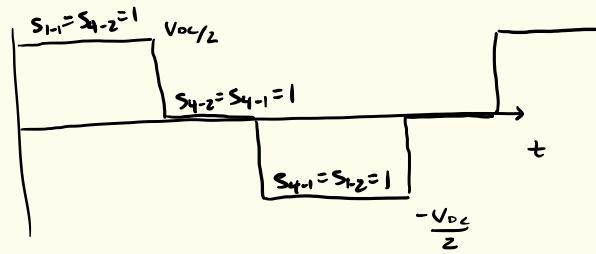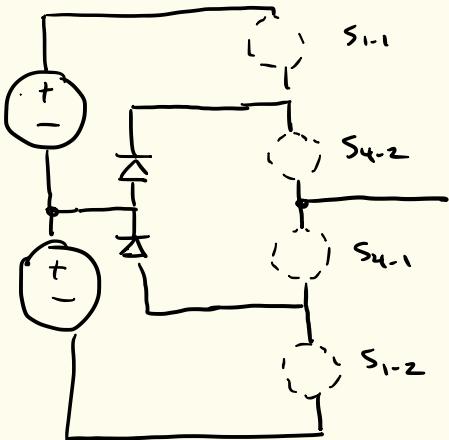
Full Circuit and output voltage trajectory




$$S_{1-1} + S_{4-1} = 1$$

$$S_{1-2} + S_{4-2} = 1$$

Switching Strategy for 3-level

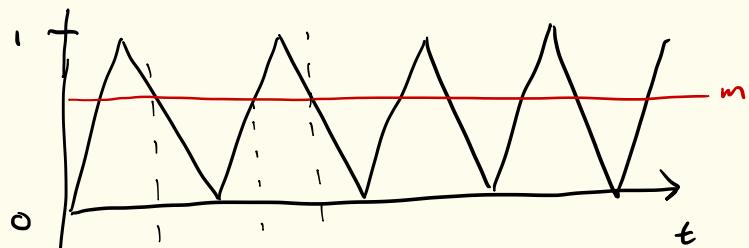

\Rightarrow unipolar triangular

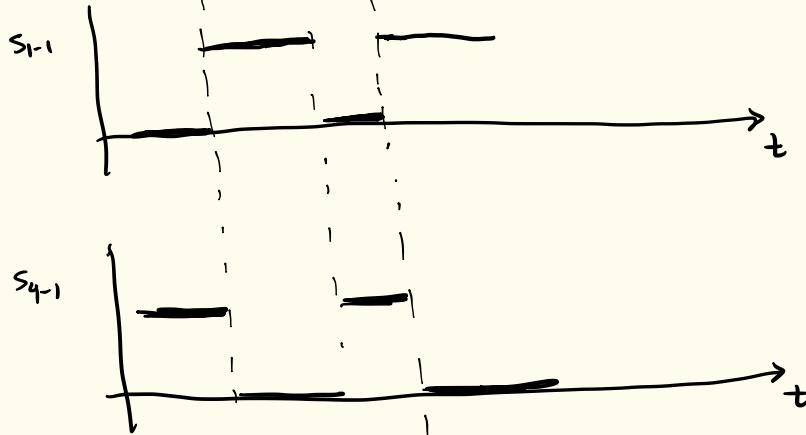

$$M > \text{carrier} \Rightarrow S_{1-1} = 1$$



$$S_{4-1} = 0$$

$$M < \text{carrier} \Rightarrow S_{1-1} = 0$$

$$S_{4-1} = 1$$

Switching S_{1-2} and S_{4-2}
is identical, except we
compare $-m$ to carrier.

What voltage waveform will we get?

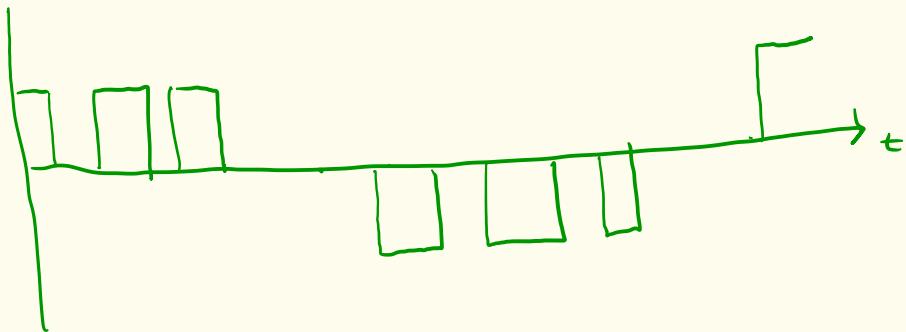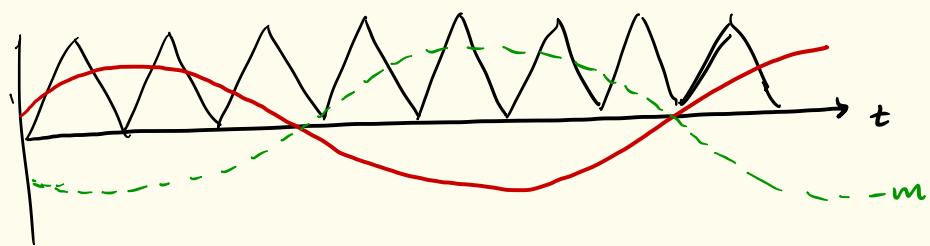


[first draw
black and red,
then after
asking stdu abt
it, draw top
green. Then
have class
think and
draw bot.
green.]

Fortunately the averaged model is simple!

$$\bar{V}_t(t) = \frac{v_{xc}}{z} m(t).$$

Same as 2-level!

3 phase architecture

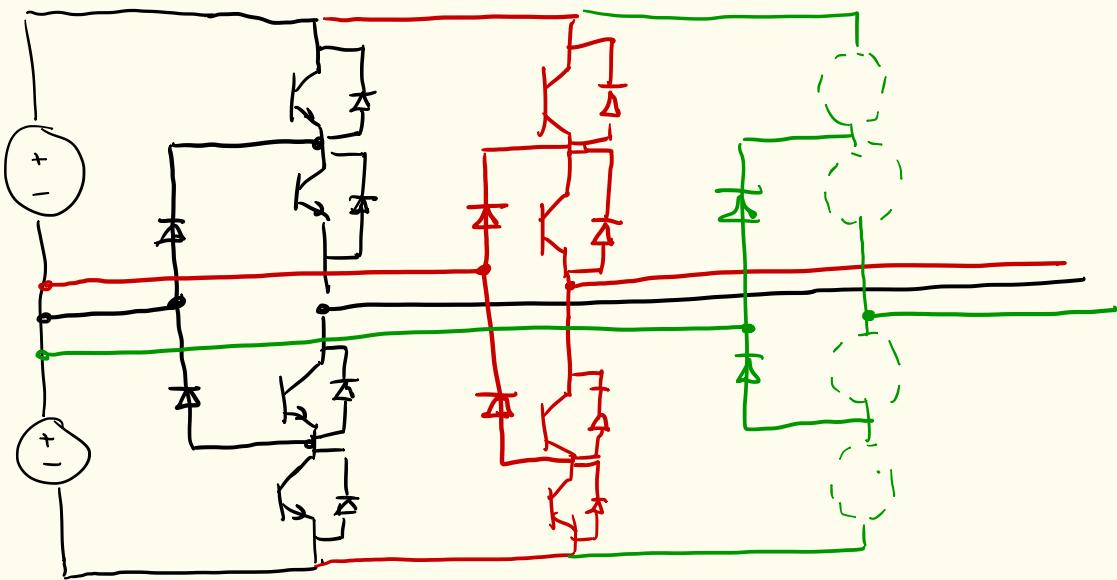




m_a, m_b, m_c are $\frac{2\pi}{3}$ apart.

Comments on Neutral point current

- Three phases drink from this well, so current always is DC plus harmonics in multiples of 3.
- With some work you can show $0.51 \hat{m} i \leq \hat{i}_{np} \leq 0.76 \hat{m} i$
 - ↑ amplitude of $m(t)$, oscillating $\odot \omega$.
 - ↑ ac current amplitude (per phase)

Example 6.1 from text:


→ $\frac{\pi}{2}$ phase shift

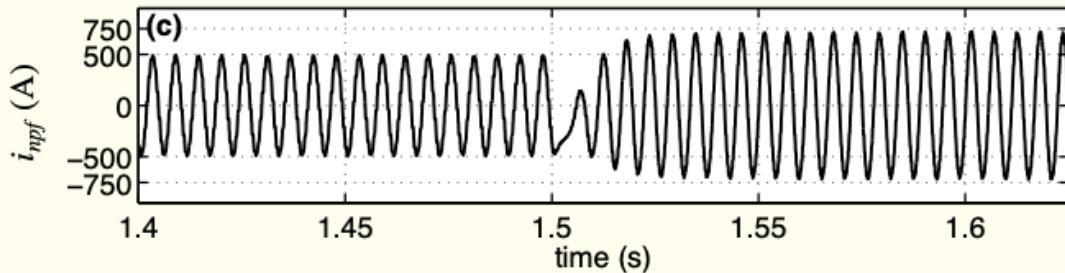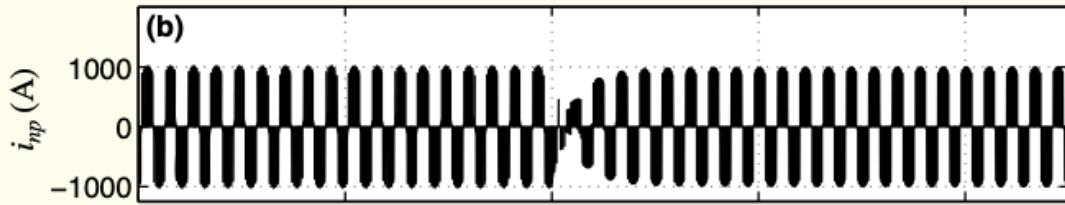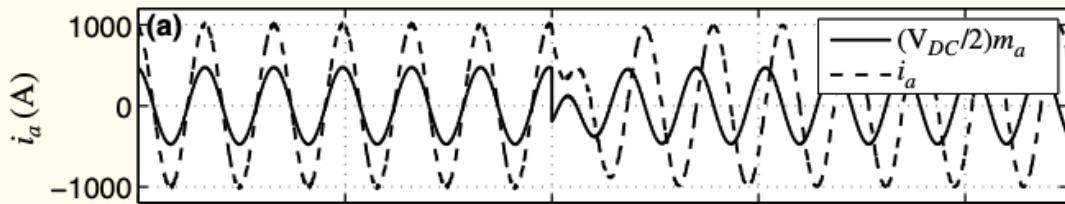

↔ all real power to AC → ← all reactive to AC →

Unifying 2-level 3 ϕ and 3-level NPC 3 ϕ .

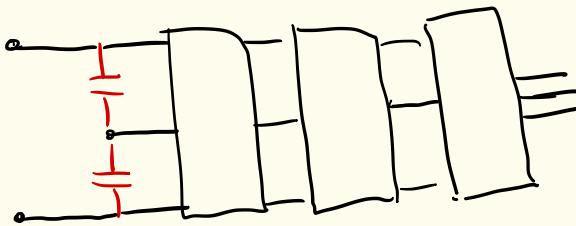- Though switching architecture and control sequences differ...
 - ... These two architectures produce the same filtered output.
- Furthermore, if we drop in a capacitor on the dc side of a 3-level:



... then one can also show the dc currents are the same for both configurations